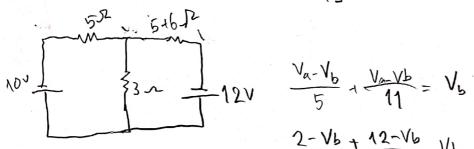


$$\frac{V_{01} \cdot V_{b}}{4} \cdot \frac{V_{01} \cdot V_{b}}{9} = \frac{V_{b}}{2}$$

$$2 - \frac{V_{b}}{5} + 2,25 - \frac{V_{b}}{4} = \frac{V_{b}}{2}$$

$$V_{b} = 4,25.20 = 4,47$$




$$\frac{V_{a}-V_{b}}{5} + \frac{V_{a}-V_{b}}{11} = V_{b}$$

$$\frac{2-V_{b}}{5} + \frac{12-V_{b}}{11} = V_{b}$$

$$\frac{34}{41} = \frac{7116}{55} = ) Vb = \frac{34.55}{41.71}$$
  
 $V_b = 2.4V$ 

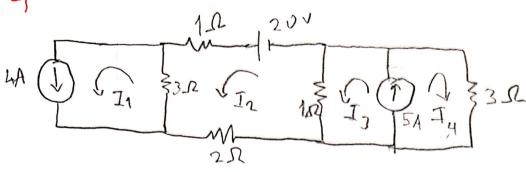=) 
$$I_{10} = -0.8 A$$
  
 $I_{20} = 2.3 A$   
 $I_{30} = -1.2 A$   
 $I_{40} = 1.1 A$   
 $I_{50} = 0.35 A$ 





$$20 = 7I_{2} - 3I_{1} - I_{3}$$

$$4 = I_{1} - I_{2}$$


$$5 = I_{3} - I_{2}$$


$$T_1 = \begin{bmatrix} 20 & 7 & -1 \\ \frac{1}{5} & -1 & 1 \\ -3 & = 16.33 \end{bmatrix}$$


$$det(I) = \begin{vmatrix} \frac{1}{3} & \frac{7}{4} & -1 \\ 0 & -1 & 0 \end{vmatrix} = 4 - 7 = -8$$

$$\frac{1}{2} = \begin{vmatrix} \frac{1}{3} & \frac{20}{4} & -1 \\ 0 & \frac{5}{3} & 1 \end{vmatrix} = 12,333 \text{ A}$$

$$\frac{7}{4}$$

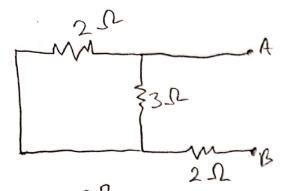

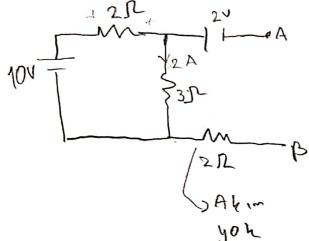

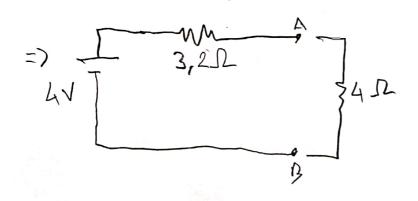

$$\overline{I_{4x}} = \frac{4}{7,2}$$

$$= \overline{I_{4x}} = 0,56A$$